

## X2Y to replace a **Common Mode Choke**

### 1) Common mode choke – basic reminder/recap

- Ideal Common Mode Choke

An ideal Common Mode Choke would let a differential signal go through with no attenuation, while it would completely block a common signal:

Differential signal:




Common signal:



- Advantage of a Common Mode Choke

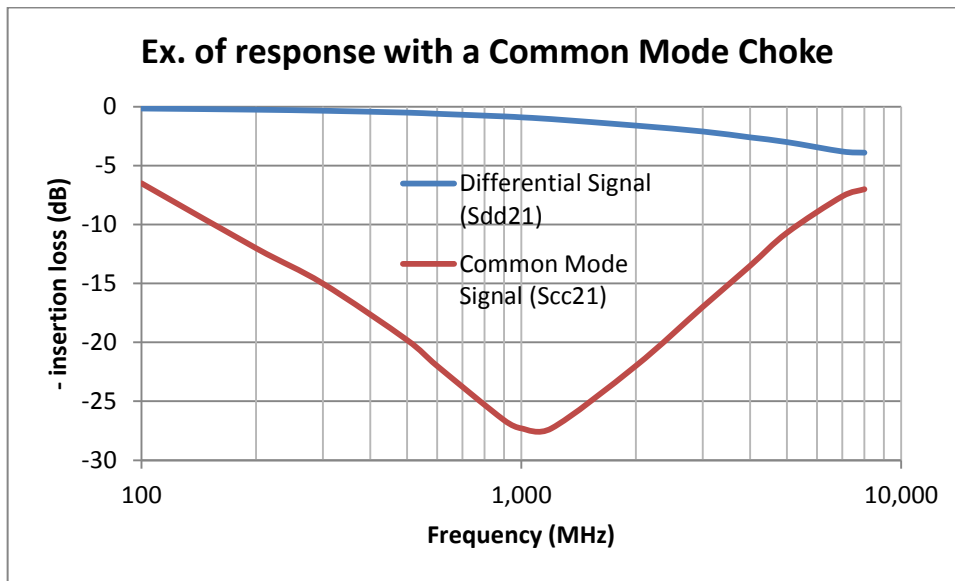In many cases, a Common Mode Choke can reject a common mode noise even when it is in the same frequency range as the differential signal we want to pass.




*In this case, a differential signal at 1GHz would have about 1dB loss (blue curve), while a common mode signal at 1GHz would have about 27 dB rejection (red curve)*

- Technical Issues with a CMC
  - The CMC is mounted in series, hence DC current limitation and power consumption.
  - Introduction of new noise due to windings that are never identical for each line.
  - Common noise rejection gets to 40 dB at the very best.
  - In most cases, need to add other components (Cy caps, Cx caps, feed-through, Pi filters, etc.) to improve performance.
  - Assembly management, especially for large sizes.

- Other issues

High cost, long lead-time, big size, weight, sensitive to vibrations, narrow temperature range...

2) X2Y component - recap

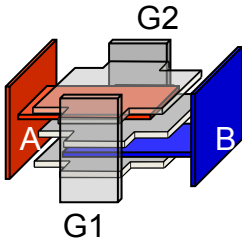

- Field shielding
- Balanced shunt impedance
- H-field cancellation (lower ESL)
- Reduction of mounted inductance\*


**\*When properly laid out** (see paragraph 6), the X2Y component provides great performances.

However, the X2Y will not be satisfactory if the differential signal is in the same frequency range as the common mode signal: Scc21 and Sdd21 are somewhat similar for an X2Y, contrary to a Common Mode Choke (see previous paragraph).


### 3) Performance comparison

PCB: 60-mil thick FR4

	Type	Size (mm)			Max DC Current Rating (A)	Max DC Resistance ( $\Omega$ )
		W	L	T		
C3	X2Y	3.2	1.6	1.27	N/A	0
L1	DC choke	7	6	3.5	4	0.015
L2	DC choke	12	11	6	8	0.06
L5	DC choke	12	11	6	6	0.014
L6	DC choke	5	5	4.5	1.4	0.85
L7	DC choke	9	7	4.5	5	0.01
L8	DC choke	4.7	4.5	2	2.6	0.05
L9	DC choke	15	13	6	10	0.004

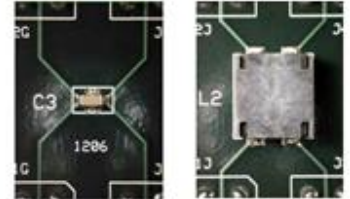

**SCC21 Common Mode Rejection**

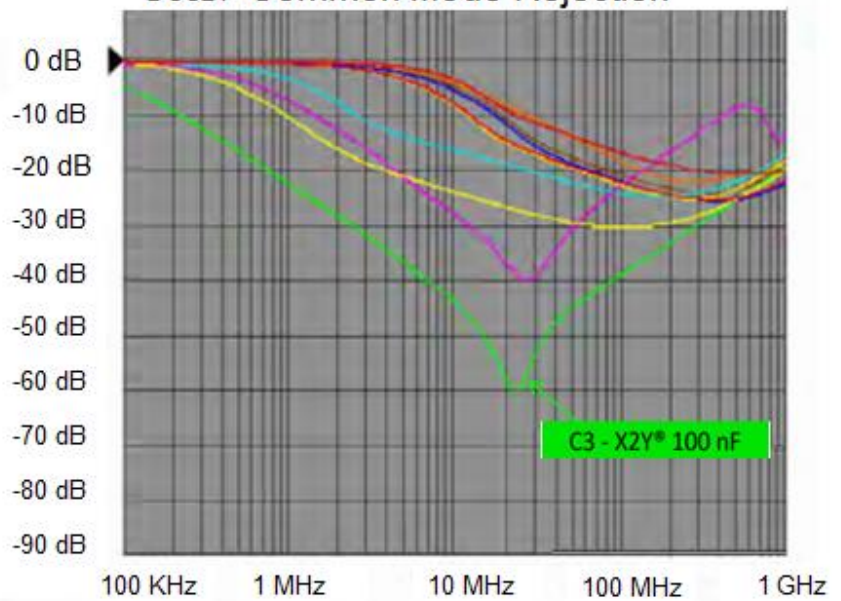


#### 4) Selection of the value of X2Y


X2Y component can be easily selected to filter EMI, based on:

- Required signal pass-band => sets maximum cap. Value
- Required noise stop band and minimum rejection => sets min value
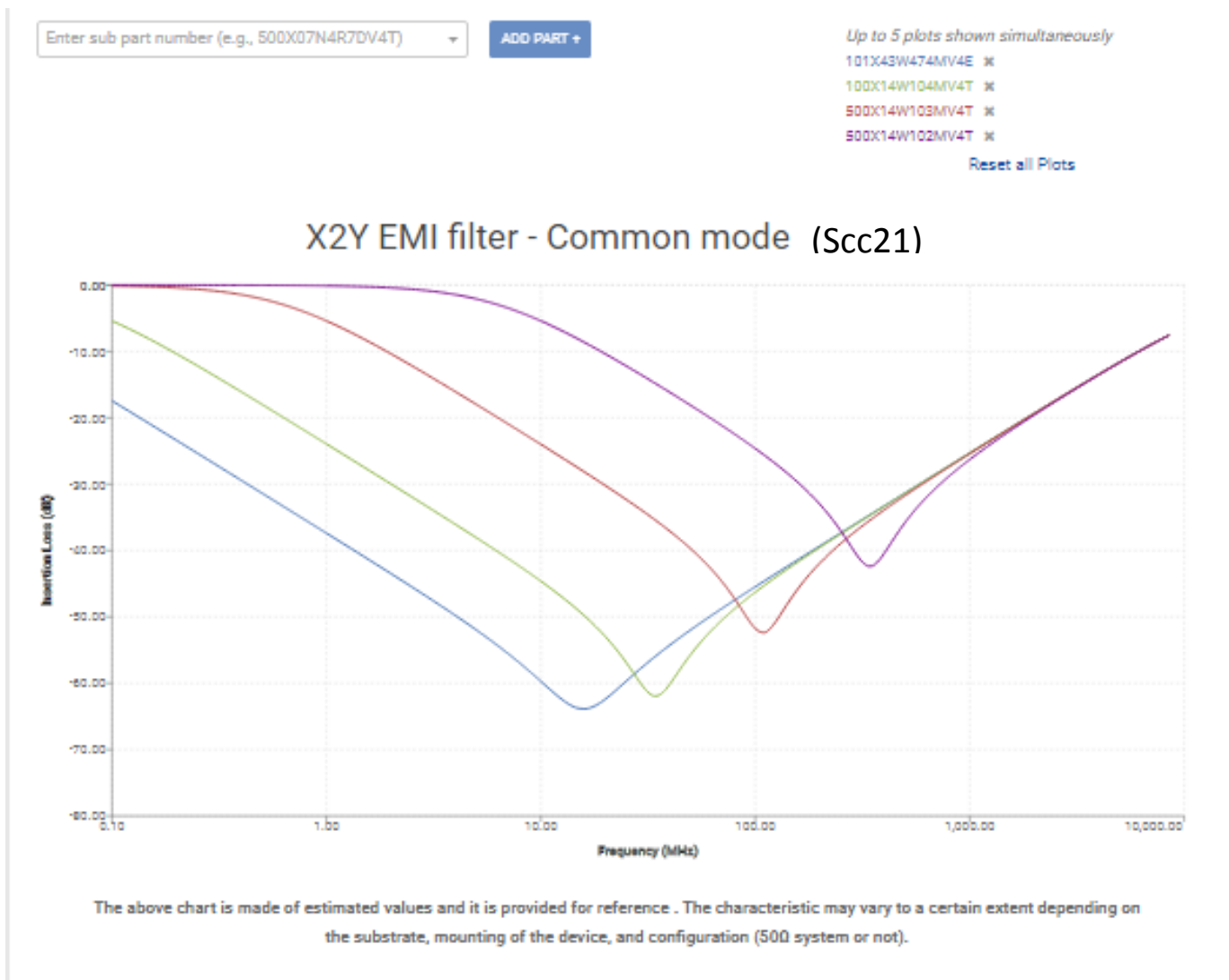
<https://s21plotter.johansondielectrics.com/>



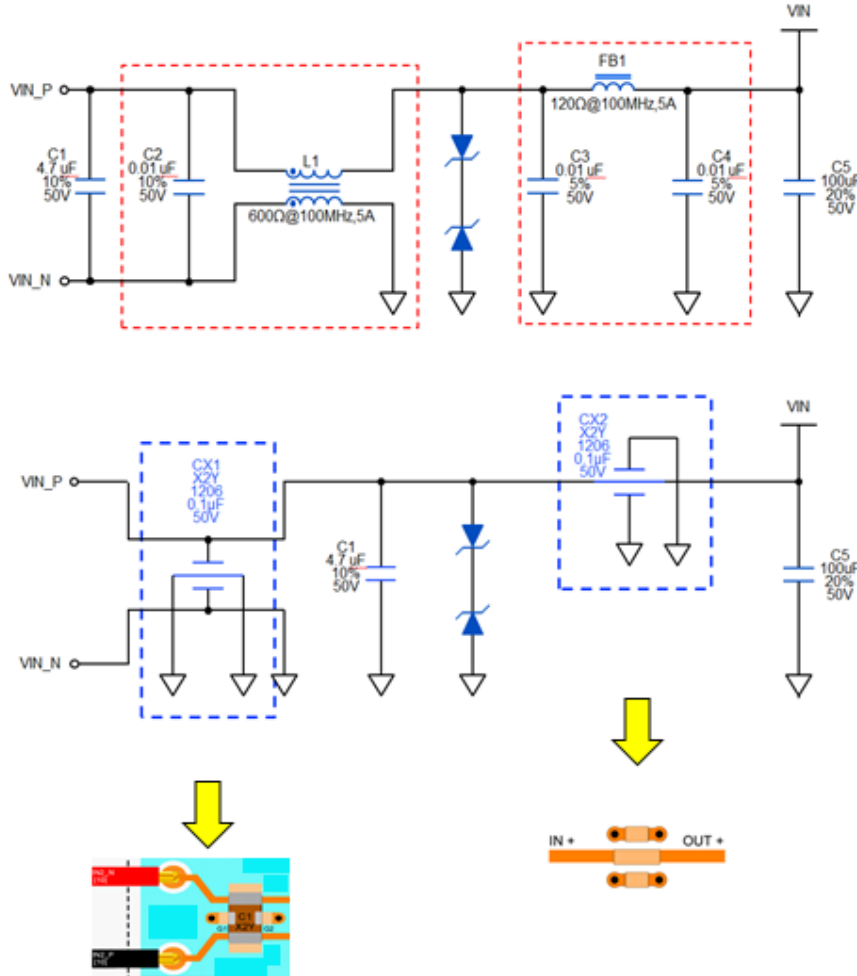5) Example: replacement of CMC + Pi filter with X2Y



6) Layout guidelines

To get the best performances of the X2Y component, it is important to follow our layout recommendations:

<https://www.johansondielectrics.com/downloads/jdi-x2y-pcb-design-guide.pdf>