




## X2Y<sup>®</sup> FPGA SerDes Bypass

Simplified design and improved performance using X2Y<sup>®</sup> capacitors w/ Altera StratixII GX SerDes

Steve Weir, Consultant with Teraspeed<sup>®</sup> Consulting Group LLC and X2Y Attenuators, LLC, has more than 20 years of experience in the Electronics Industry, holds 17 U.S. patents and has architected a number of packet and TDM switching products. Steve has participated as a TecPanelist at several DesignCon Symposiums and authored numerous technical papers on the subject of bypass capacitor application for PDN design. Steve is a frequent contributor to the Si-List message reflector, dedicated to signal and power integrity.

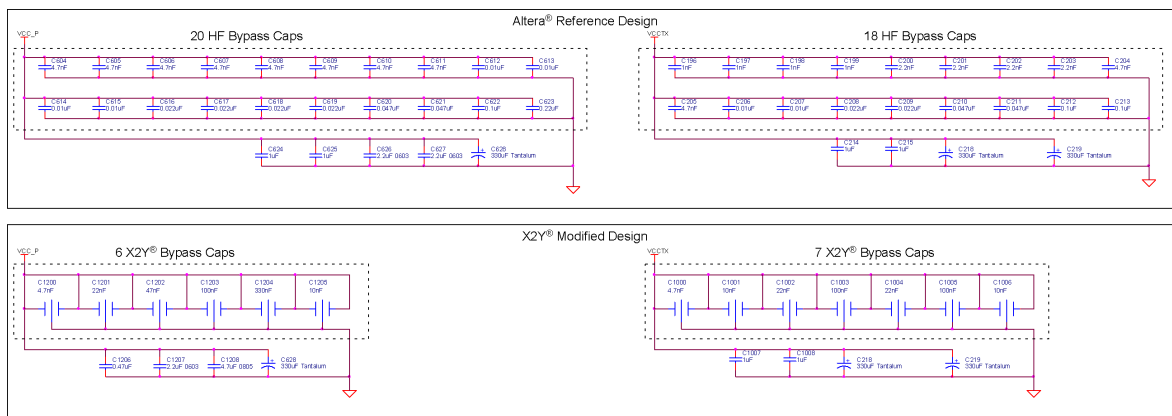
## Comparative Bypass Networks

- SERDES transmit power supplies:
  - 13 X2Y<sup>®</sup> Capacitors replace 38 0402 caps
  - Plane inductance saturation for each supply is achieved w/ 2 X2Y<sup>®</sup> capacitors




# X2Y v. MLCCs

MLCC Design


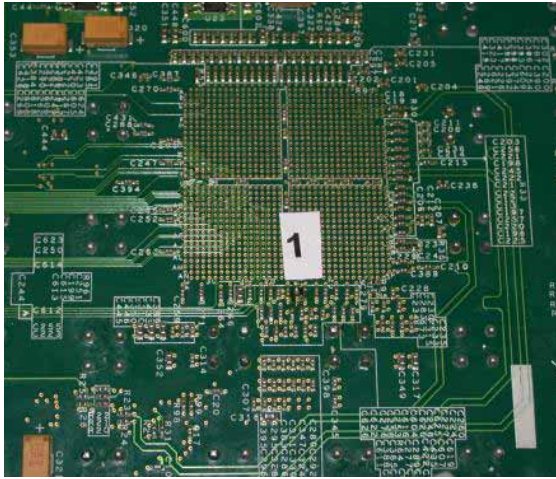


X2Y® Design

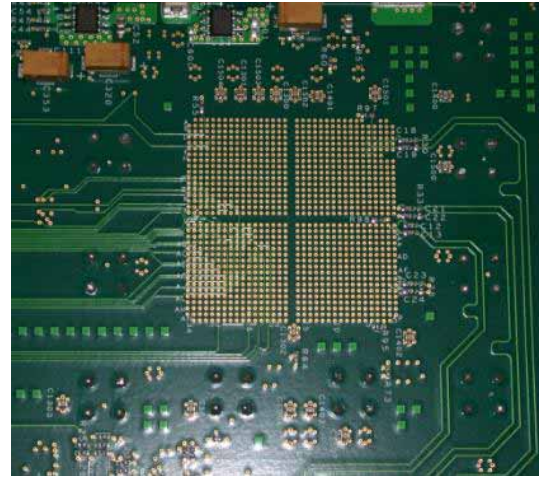

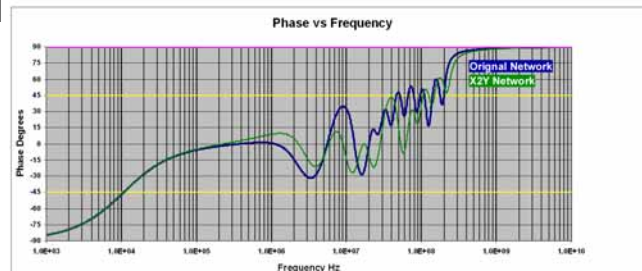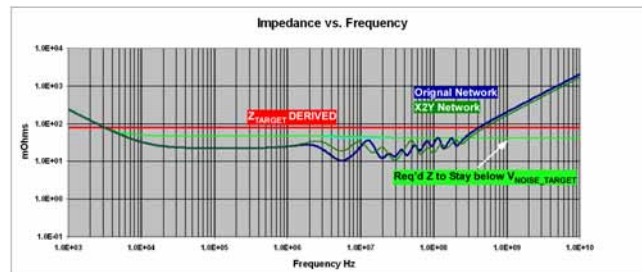
# Transmit Analog: VCCH

- X2Y® Design
  - 2 x 330uF tantalum caps + 2 MLCCs + 7 X2Y®
  - 1D < 80mOhms equivalent resistive to 250MHz
    - Ignores spatial effects and IC parasitics
    - Spatial effects dominate above 10MHz


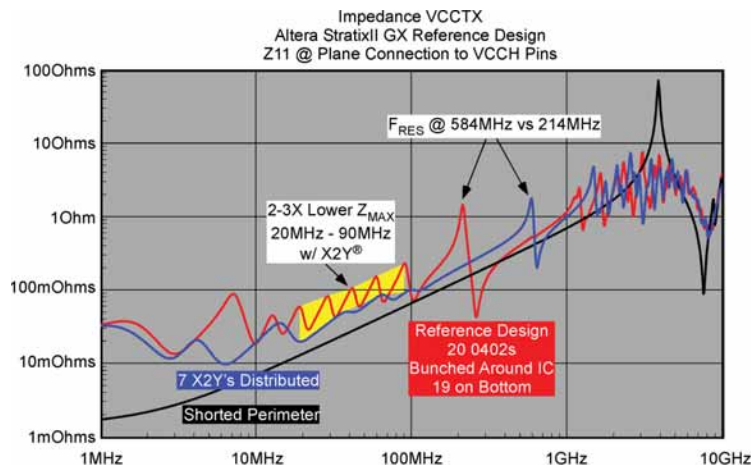
# Impedance Comparisons w/o IC

- 2-3X lower impedance 20MHz-100MHz w/ 7 caps instead of 20
  - >2.5:1 Higher  $F_{RES}$
  - 2.5:1 reduction in Q




10/8/2008

© X2Y Attenuators, LLC

6

# Original VCCTX and X2Y® Networks
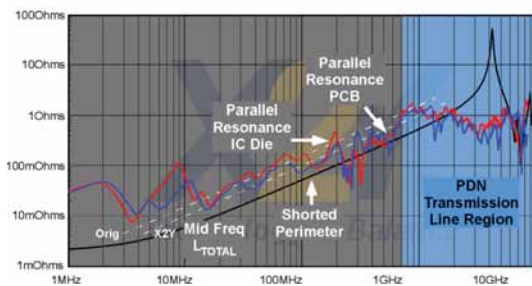
## Measured VCCTX Networks vs Simulated Shorted Perimeter




- Original network, FDTIM
  - $L_{BYPASS}$  decreases with increasing freq.
  - Near 20MHz about  $L_{TOTAL}$  about 220pH
  - Die / bypass PRF near 200MHz
  - Bypass / PCB PRF near
- X2Y® network selective zeroes
  - Lower  $L_{BYPASS}$  @ 20MHz up
  - Zero for Die / bypass PRF
  - Zero for PCB / bypass PRF

10/8/2008

© X2Y Attenuators, LLC

7

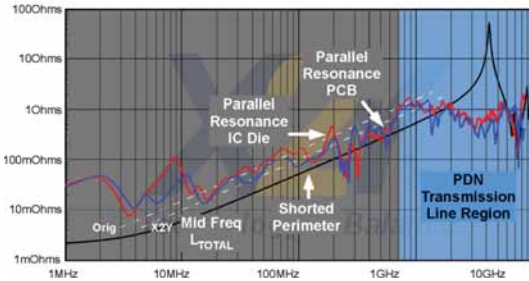
## Measured VCCTX Networks vs Simulated Shorted Perimeter



- Original network
  - @ relatively low PRF
- X2Y® Network
  - Lower distributed L of 6/7
  - X2Y® caps raises to 580MHz
  - Suppressed w/ single 100pF rated X2Y®
    - Good suppression w/ conventional caps difficult due to high Q
  - Measured results, PRF completely suppressed

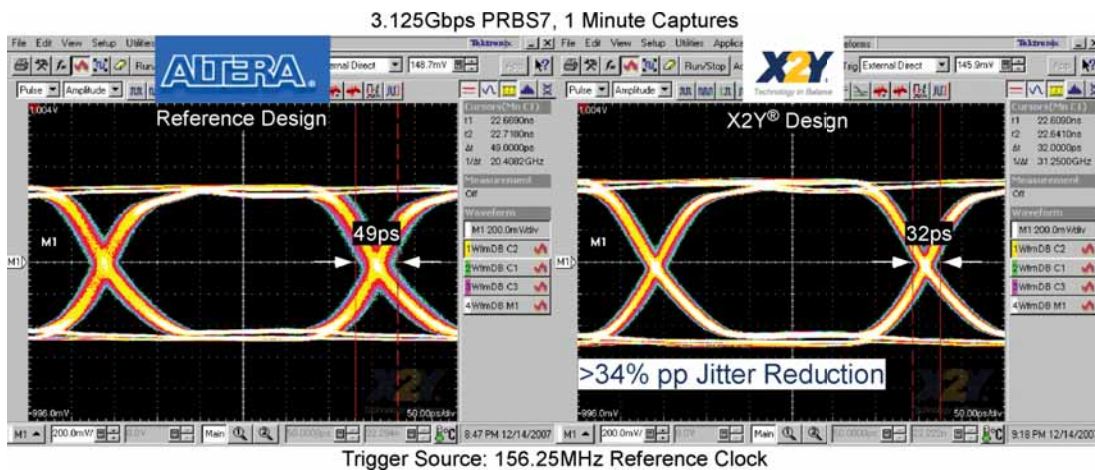
# 3.125Gbps Performance PRBS7

- X2Y® Reduces jitter to 32ps p-p jitter
  - vs 49ps in reference design


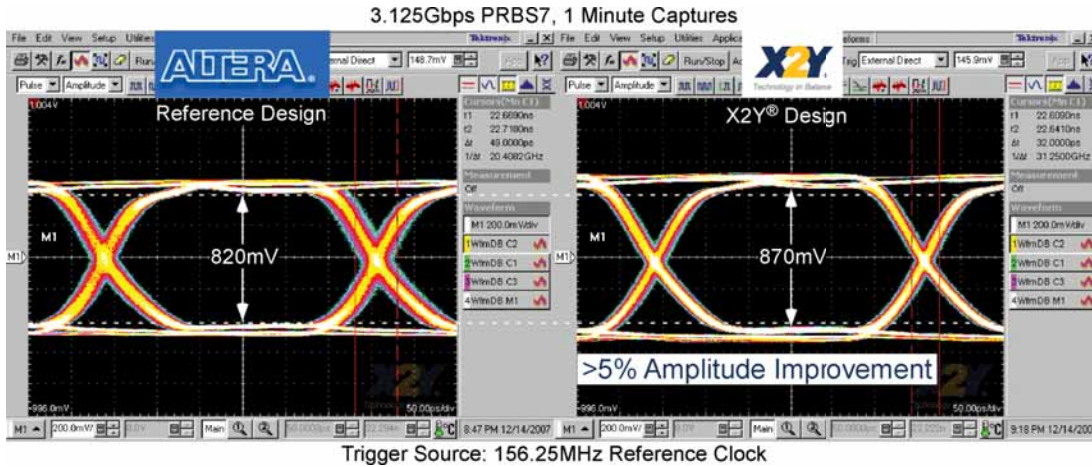
# 3.125Gbps Performance PRBS7

- X2Y® improves better eye amplitude >5%
  - 870mV pp @ sample point vs 820mV pp reference




10/8/2008

© X2Y Attenuators, LLC

10
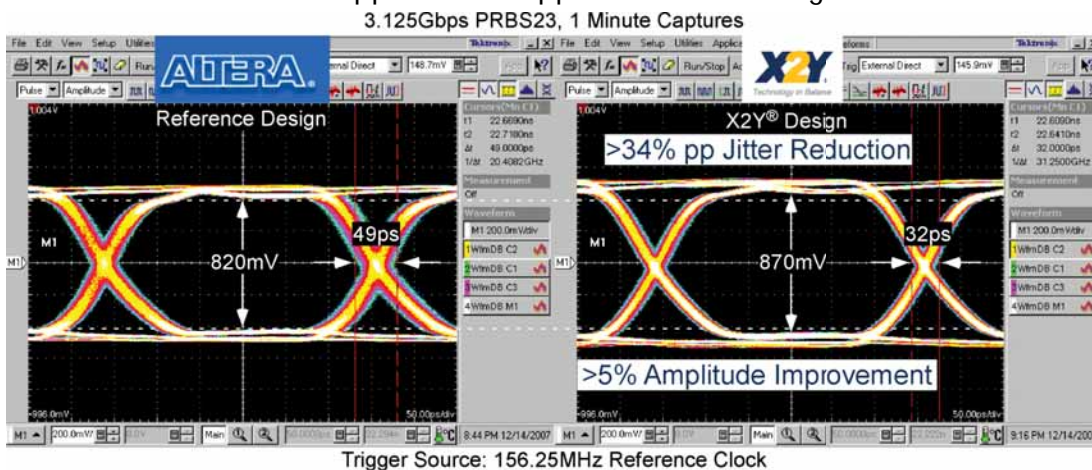
# 3.125Gbps Performance PRBS23

- Shows same improvements in jitter and eye amplitude:
  - X2Y® 32ps p-p jitter vs 49ps in reference design
  - X2Y® 870mV pp vs 820mV pp in reference design



10/8/2008

© X2Y Attenuators, LLC

11